

SPRING 2016
CSE251: Electronic Devices and Circuits
Assignment # 03

Submission Deadline: Monday, 21st March 2016

1. Sketch and Explain **Input** and **Output** characteristics curves for **Common-Base**, **Common-Collector** and **Common-Emitter**.

2. ‘ **Electronic Devices and Circuits**’ -David A. Bell (Fourth Edition):
Chapter 05: (Exercise (Pg. 168-171))

5-9, 5-11, 5-12, 5-13, 5-17, 5-18, 5-19, 5-29, 5-30, 5-33, 5-34, 5-42